

LMM104RM0 Regulated 48V - 12V Intermediate Bus Converter

1 Features

- · Supports wide input voltage range: 40V to 60V
- · Rated output power: 1.6kW
- Peak power: 2.4kW (< 200ms)
- · Fully regulated output voltage: 12V
- Typical peak efficiency: 97.6% at 48V and 97.6% at 54V
- Typical full load efficiency: 96.8% at 48V and 96.6% at 54V
- Non-isolated design
- Typical switching frequency: 200kHz
- Supports PMBus communication
- · Fully protected:
 - Input UVLO
 - Input OVP
 - Output OVP
 - Output OCP
 - OTP
- Typical output voltage ripple: 100mV
- · Heat spreader for top side cooling
- Mechanical dimensions: 58.4mm × 36.8mm × 15.5mm

2 Applications

- Data center intermediate bus converters (IBCs)
- Power distribution board (PDB) for servers and communications
- DC-DC converters


3 Description

The LMM104RM0 module is an evolution within the TI intermediate bus converters family. This module is a high-efficiency, regulated, non-isolated, 1.6kW thermal design power (TDP), in a standard quarter-brick footprint. The modular design provides a high-power density power conversion from 48V bus to a regulated 12V output, with options for parallel connection with multiple modules and current sharing through active-current control.

Package Information

PART NUMBER	PACKAGE	PACKAGE SIZE(1)
LMM104RM0		58.4mm × 36.8mm × 15.5mm

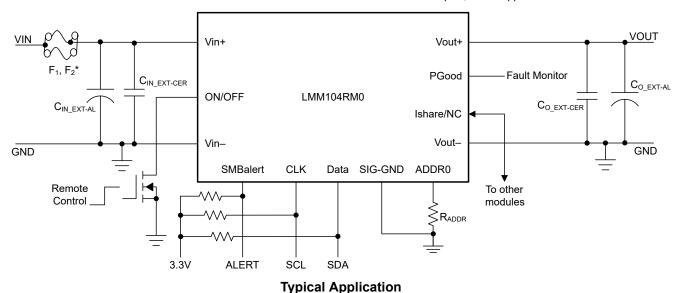(1) The package size (length × width × height) is a nominal value and includes pins, where applicable.





4 Device and Documentation Support

TI offers an extensive line of development tools. Tools and software to evaluate the performance of the device, generate code, and develop solutions are listed below.

4.1 Receiving Notification of Documentation Updates

To receive notification of documentation updates, navigate to the device product folder on ti.com. Click on *Notifications* to register and receive a weekly digest of any product information that has changed. For change details, review the revision history included in any revised document.

4.2 Support Resources

TI E2E[™] support forums are an engineer's go-to source for fast, verified answers and design help — straight from the experts. Search existing answers or ask your own question to get the quick design help you need.

Linked content is provided "AS IS" by the respective contributors. They do not constitute TI specifications and do not necessarily reflect TI's views; see TI's Terms of Use.

4.3 Trademarks

TI E2E[™] is a trademark of Texas Instruments.

All trademarks are the property of their respective owners.

4.4 Electrostatic Discharge Caution



This integrated circuit can be damaged by ESD. Texas Instruments recommends that all integrated circuits be handled with appropriate precautions. Failure to observe proper handling and installation procedures can cause damage.

ESD damage can range from subtle performance degradation to complete device failure. Precision integrated circuits may be more susceptible to damage because very small parametric changes could cause the device not to meet its published specifications.

4.5 Glossary

TI Glossary

This glossary lists and explains terms, acronyms, and definitions.

Submit Document Feedback

Copyright © 2025 Texas Instruments Incorporated

IMPORTANT NOTICE AND DISCLAIMER

TI PROVIDES TECHNICAL AND RELIABILITY DATA (INCLUDING DATA SHEETS), DESIGN RESOURCES (INCLUDING REFERENCE DESIGNS), APPLICATION OR OTHER DESIGN ADVICE, WEB TOOLS, SAFETY INFORMATION, AND OTHER RESOURCES "AS IS" AND WITH ALL FAULTS, AND DISCLAIMS ALL WARRANTIES, EXPRESS AND IMPLIED, INCLUDING WITHOUT LIMITATION ANY IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE OR NON-INFRINGEMENT OF THIRD PARTY INTELLECTUAL PROPERTY RIGHTS.

These resources are intended for skilled developers designing with TI products. You are solely responsible for (1) selecting the appropriate TI products for your application, (2) designing, validating and testing your application, and (3) ensuring your application meets applicable standards, and any other safety, security, regulatory or other requirements.

These resources are subject to change without notice. TI grants you permission to use these resources only for development of an application that uses the TI products described in the resource. Other reproduction and display of these resources is prohibited. No license is granted to any other TI intellectual property right or to any third party intellectual property right. TI disclaims responsibility for, and you will fully indemnify TI and its representatives against, any claims, damages, costs, losses, and liabilities arising out of your use of these resources.

TI's products are provided subject to TI's Terms of Sale or other applicable terms available either on ti.com or provided in conjunction with such TI products. TI's provision of these resources does not expand or otherwise alter TI's applicable warranties or warranty disclaimers for TI products.

TI objects to and rejects any additional or different terms you may have proposed.

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265 Copyright © 2025. Texas Instruments Incorporated